Downloaded from www.artofhacking.com

TAP

MAR-APR 1980 NO.62

Milo Foneblll's Automatic Blue Box Explained
by Lavelster

Advantages of Milo's Box
1. Can hold 5 10 digit numbers.
2. Each number is outpulsed at the proper rate at the touch of a single key.
3. The current drain is very low. When not pulsing the battery drain is only 40 microamps. A single 9 volt alkeline battery will power it for a year of on time, unlike Peter Pirer's programmable box (TAP # 56) which takes two 9V batteries and pulls 20ma in standby

Disadvantages of Milo's Box
1. The box is complex.
2. Because of its complexity it is bulkier than the usual manual box.

The enclosed schematic is of a working Milo Foneblll 88. It took one hell of a lot of study to figure it out from Milo's writeup. I'll describe how it works in 3 sections: 1. Number entry; 2. Playing back the numbers, or RUN; 3. Clearing the Box.

1. Number entry. Assume the box has been cleared and a 1 is in all 64 bits of each register. I'll get to the reason for this later. The switch enabling the keyboard is closed. You assure that the KP key is connected thus 1100 and 1700 go low. A "0" (0 is low, 1 is high)is placed on pin 15 (Data In) of IC 0 & 12 but the data is not entered yet. At the same timeith 4 or 1054 and pin 15 of 1064 (on which drives pin 1) of IC1042 low. This in turn makes pin 10 of all the shift registers low. Pins 1064 and 2016B. This sets the shift registers in data entry mode. Meanwhile charge in leading edge of 0% through R14 and after about 5ms20 goes high and KP goes low. This delay is to allow for contact bounce in the keyboard switches. 40 high drives pin 2 (clock input) of all the shift registers high. The data present at pin 15 of all the shift registers is now entered. KP went low after 50ms which, through 1064, 1074A-F, and 1012 AP turns on the solid sanitizer (1076E) giving an audible click and lights the pulsing gate indicator LED. The 1k2 stays lit as long as the gate is sustained.

Let us repeat, a 0 is entered into the 1100 and 1700 shift registers and a 1 is entered in the 700, 900, 1500, and 1500 shift registers when KP is pressed on the keyboard.

The Schmitt triggers (2016Far) reduce the 4047 used in Milo's box.I could not get the 4047 to work in this application. Besides the 2016's Schmitt trigger is cheaper. Note also that the P gate indicator driver should be a nonn-inverting buffer and not an inverting buffer as Milo shows it.

The 4011 shift register, unlike other CMOS IC=, has a large clock level capacitance (5pf) so I play safe and drive them with 5 inverting buffers rather than 1 as Milo does. The 1k2 stays lit as long as the gate is sustained